

# Lava 4

brief info for TH exam

Code for this lecture provided in EFile12.hs  
on the Assignments page.

The file DrawPP12.hs is for drawing pictures.


# Q: How can we speed this up?

```
adder0 :: [(Bit, Bit)] -> ([Bit], Bit)
adder0 abs = row fullAdd (low,abs)
```

# Q: How can we speed this up?

```
adder0 :: [(Bit, Bit)] -> ([Bit], Bit)
adder0 abs = row fullAdd (low,abs)
```

row is a connection pattern

 


# A: Compute carries separately


will show a sequence of functions that each  
have same behaviour

# Some useful stuff


$$\text{fsT } f = (f \text{ -|} \text{ id})$$

 

$$\text{snD } f = (\text{id} \text{ -|} \text{ } f)$$

 

 
$$\begin{aligned} \text{fb} &:: ((a,b) \rightarrow c) \rightarrow (a,b) \rightarrow ((a,b),c) \\ \text{fb } \text{circ } ab &= (ab, \text{circ } ab) \end{aligned}$$


 
# another view of full adder

`fullAdd1 :: (Bit,(Bit,Bit)) -> (Bit,Bit)`

`fullAdd1 = snD gpC ->- fb carryC ->- fsT sumC`



gpC :: (Bit, Bit) -> (Bit, Bit)  
gpC (a, b) = (a <&> b, a <#> b)

sumC :: (Bit, (Bit, Bit)) -> Bit  
sumC (cin, (\_, p)) = cin <#> p


carryC :: (Bit, (Bit, Bit)) -> Bit  
carryC (cin, (g, p)) = g <|> (cin <&> p)


 
# Why this structure?

carryC can be tailored to have short delay from carry in to carry out


Carrys can be computed in parallel (see later)




# Can we rewrite this?

```
adder1 :: [(Bit, Bit)] -> ([Bit], Bit)  
adder1 abs = row fullAdd1 (low,abs)
```

# One row

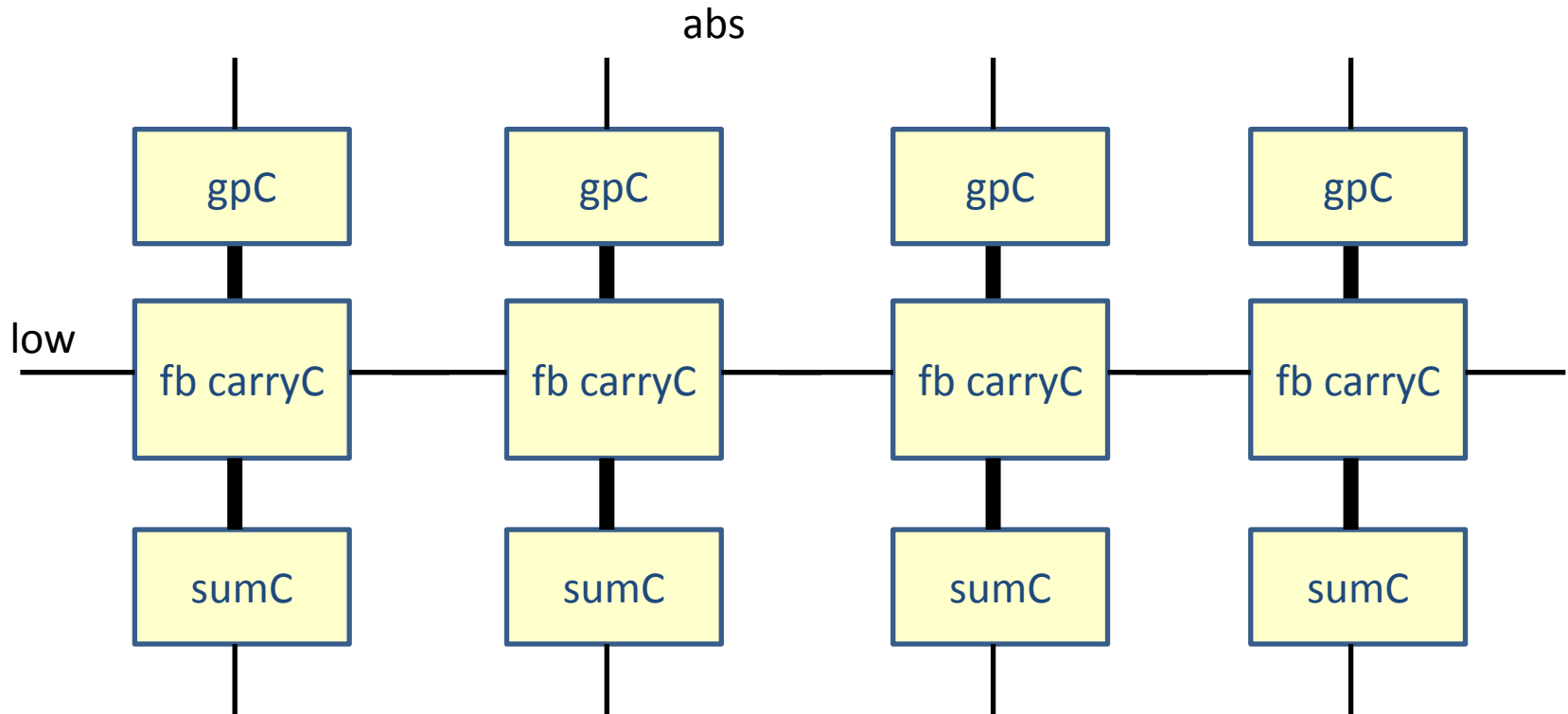

# Same as two maps and a row

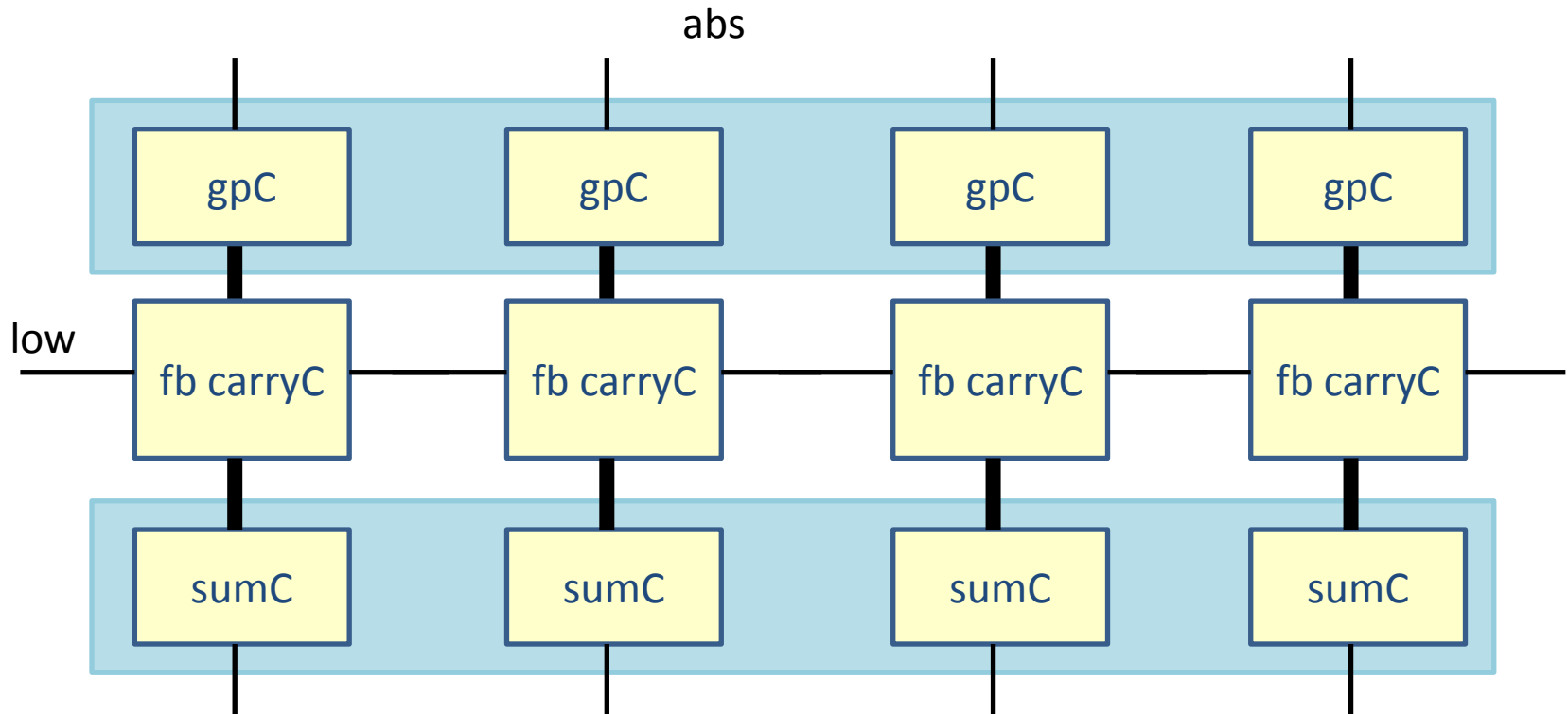


# Two maps and a row

```
adder2 :: [(Bit, Bit)] -> ([Bit], Bit)
adder2 abs = (ss, cout)
  where
    gps      = map gpC abs
    (rs, cout) = row (fb carryC) (low, gps)
    ss       = map sumC rs
```

# Isolate the carry chain

$\text{fb} :: ((a,b) \rightarrow c) \rightarrow (a,b) \rightarrow ((a,b),c)$   
 $\text{fb circ ab} = (\text{ab}, \text{circ ab})$


$\text{fb carryC}$

 

# Isolate the carry chain

$f1 :: ((a,b) \rightarrow c) \rightarrow (a,b) \rightarrow (a,c)$   
 $f1 \text{ circ } (a,b) = (a, \text{circ } (a,b))$

$f1 \text{ carryC}$

 


# slight reorg

```
adder3 :: [(Bit, Bit)] -> ([Bit], Bit)
adder3 abs = (ss, cout)
  where
    gps      = map gpC abs
    (cs, cout) = row (f1 carryC) (low, gps)
    rs       = zip cs gps
    ss       = map sumC rs
```



# isolated the carry calculation

 


# Remember

We can replace linear array by binary tree for associative operator

Similar game can be played for row

# isolated the carry calculation

 

But carryC can't be associative:


```
f1 carryC :: (Bit, (Bit, Bit)) -> (Bit, Bit)
```

(Need type  $(a,a) \rightarrow a$ )


# Brent and Kung's insight

If we can find an associative operator that still computes the same thing when placed in a row, then we will be able to do much better than a linear array!

# enhance carryC

 

# enhance carryC

 

# enhance carryC

```
dotOp :: ((Bit, Bit), (Bit, Bit)) -> (Bit, Bit)
```

```
dotOp ((g1, p1), (g2, p2)) = (carryC (g1, (g2, p2)), p1 <&> p2)
```

# enhance carryC

```
dotOp :: ((Bit,Bit), (Bit,Bit)) -> (Bit,Bit)
dotOp ((g1,p1), (g2,p2)) = (carryC (g1, (g2,p2)), p1 <&> p2)
```

Need also to compensate for this change so that the entire circuit retains its function




# enhance carryC

```
adder4 :: [(Bit, Bit)] -> ([Bit], Bit)
adder4 abs = (ss,cout)
  where
    gps      = map gpC abs
    (cs,cout) = (row (f1 dotOp) ->- (map fst -|- fst)) ((low,high), gps)
    rs       = zip cs gps
    ss       = map sumC rs
```


# enhance carryC

```
adder4 :: [(Bit, Bit)] -> ([Bit], Bit)
adder4 abs = (ss, cout)
  where
    gps      = map gpC abs
    (cs, cout) = (row (f1 dotOp) ->- (map fst -|- fst)) ((low, high), gps)
    rs       = zip cs gps
    ss       = map sumC rs
```

# New situation (associative op.)

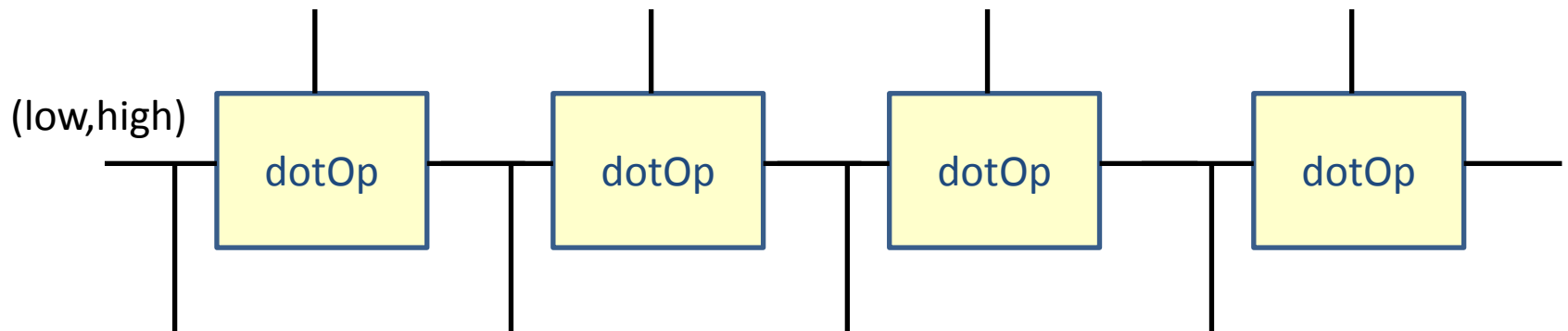

# New situation (associative op.)

 

Matches the famous Prefix Problem!

# Prefix

Given inputs  $x_1, x_2, x_3 \dots x_n$

Compute  $x_1, x_1 * x_2, x_1 * x_2 * x_3, \dots, x_1 * x_2 * \dots * x_n$

Where  $*$  is an arbitrary associative (but not necessarily commutative) operator

# Why interesting?

Microprocessors contain LOTS of parallel prefix circuits  
not only binary and FP adders  
address calculation  
priority encoding etc.

Overall performance depends on making them fast  
But they should also have low power consumption...

Parallel prefix is a good example of a connection pattern  
for which it is interesting to do better synthesis



# Visualizing prefix networks

Serial prefix



least

most significant

  


# Visualizing prefix networks

Serial prefix




least

most significant



 









3 more

   

# 3 more

   


# Basic building block: fan

     


type Fan a = [a] -> [a]

 
type PP a = Fan a -> [a] -> [a] -- Prefix network



 $\text{ser3} :: \text{PP a}$   
 $\text{ser3 f [a,b,c] = [a1,b2,c2]}$   
 where  
 $[a1,b1] = \text{f [a,b]}$   
 $[b2,c2] = \text{f [b1,c]}$




 $\text{f31} :: \text{PP a}$   
 $\text{f31 f [a,b,c] = [a1,b2,c2]}$   
 where  
 $[b1,c1] = \text{f [b,c]}$   
 $[a1,b2,c2] = \text{f [a,b1,c1]}$



$\text{f32} :: \text{PP a}$   
 $\text{f32 f [a,b,c] = [a2,b2,c2]}$   
 where  
 $[b1,c1] = \text{f [b,c]}$   
 $[a1,c2] = \text{f [a,c1]}$   
 $[a2,b2] = \text{f [a1,b1]}$

# Useful fan parameters

 

```
mkFan :: ((a,a) -> a) -> Fan a  
mkFan op (i:is) = i:[op(i,k) | k <- is]
```

```
pplus :: Fan (Signal Int) -- For making a prefix of additions  
pplus = mkFan plus
```

```
delFan :: Fan (Signal Int) -- For delay estimation  
delFan [i] = [i]  
delFan is = replicate n (1 + maximum is)  
  where  
    n = length is
```

```
t3 = simulate (ser3 pplus) [1,2,3]
```

```
> t3
```

```
[1,3,6]
```

```
t3d = simulate (ser3 delFan) [0,0,0]
```


```
> t3d
```

```
[1,2,2]
```

# serial prefix

```
ser :: PP a
ser _ [a]      = [a]
ser f (a:b:bs) = a1:cs
  where
    [a1,a2] = f [a,b]
    cs      = ser f (a2:bs)
```


```
> drawPP "ser" ser 8
```

 

8 lines, 7 stages, 7 operators, 2 maximum fanout.



```
> drawPP "ser" ser 8
```

 


xfig file is produced (by symbolic evaluation) + hack

8 lines


From xfig, pdf and many formats available

anout.

# Sklansky

 

# Sklansky

 

32 lines    5 stages (= minimum)    80 operators

```
skl :: PP a
skl _ [a] = [a]
skl f as = init los ++ ros'
  where
    (los,ros) = (skl f las, skl f ras)
    ros'      = f (last los : ros)
    (las,ras) = splitAt (cnd2 (length as)) as
```

```
cnd2 n = n - n `div` 2 -- Ceiling of n/2
```

# back to the adder!

```
adder4 :: [(Bit, Bit)] -> ([Bit], Bit)
adder4 abs = (ss,cout)
  where
    gps      = map gpC abs
    (cs,cout) = (row (f1 dotOp) ->- (map fst -|- fst)) ((low,high), gps)
    rs       = zip cs gps
    ss       = map sumC rs
```

if  $(cs, c) = \text{row } (f1 \text{ circ}) (e, as)$   
and  $e$  is an identity of  $\text{circ}$

then

$cs ++ [c] = e : \text{ser } (\text{mkFan } \text{circ})$

# back to the adder!

```
adder5 :: [(Bit, Bit)] -> ([Bit], Bit)
adder5 abs = (ss, cout)
  where
    gps      = map gpC abs
    (cs, cout) = (ser (mkFan dotOp) ->- unsnoc ->- (map fst -|- fst) ) gps
    rs       = zip (low:cs) gps
    ss       = map sumC rs
```

```
unsnoc as = (init as, last as)
```

# slight optimisation (remove low)

```
adder6 :: [(Bit, Bit)] -> ([Bit], Bit)
adder6 abs = (ss,cout)
  where
    gps          = map gpC abs
    (cs,cout)    = (ser (mkFan dotOp) ->- unsnoc ->- (map fst -|- fst) ) gps
    ((_,p) : gps') = gps
    rs           = zip cs gps'
    ss           = p : map sumC rs
```



BUT now we can use any prefix  
network we fancy instead of ser

and there are lots to choose from!

# Sklansky

```
adder7 :: [(Bit, Bit)] -> ([Bit], Bit)
adder7 abs = (ss,cout)
  where
    gps          = map gpC abs
    (cs,cout)    = (skl (mkFan dotOp) ->- unsnoc ->- (map fst -|- fst) ) gps
    ((_,p) : gps') = gps
    rs           = zip cs gps'
    ss           = p : map sumC rs
```

# Sklansky


```
adder7 :: [(Bit, Bit)] -> ([Bit], Bit)
adder7 abs = (ss, cout)
  where
    gps          = map gpC abs
    (cs, cout)    = (skl (mkFan dotOp) ->- unsnoc ->- (map fst -|- fst) ) gps
    ((_,p) : gps') = gps
    rs            = zip cs gps'
    ss            = p : map sumC rs
```

Size (= power consumption) and performance completely dominated by the prefix network

Could (and should) parameterise on the pattern


# Brent Kung network

> drawPP "bK" bKung 32

 


32 lines, 9 stages, 57 operators, 2 maximum fanout.

# Brent Kung: Recursive structure

 

# Ladner Fischer min. depth


> drawPP "LF0" (ladF 0) 32

 

32 lines, 5 stages, 74 operators, 17 maximum fanout.

# Ladner Fischer min. depth


> drawPP "LF0" (ladF 0) 32

 

32 lines, 5 stages, 74 on 17 maximum fanout.

Beware. Many papers and books are wrong about LF (and think it is the same as Sklansky). It is not!


# LF min depth + 1

 

32 lines, 6 stages, 62 operators, 9 maximum fanout.



# and more

 

32 lines, 6 stages, 63 operators, 5 maximum fanout.

# Problem

Find a sweet spot

LAGOM

Not too big

Not too deep

Not too much fanout

# Questions?